




# Analog and RF CMOS circuit design

Design of a fully integrated wireless power transmitter–  
Some theoretical elements

Alexandre Boyer  
*alexandre.boyer@insa-toulouse.fr*  
*www.alexandre-boyer.fr*

**2017-2018**

## Simplified operation of MOSFET

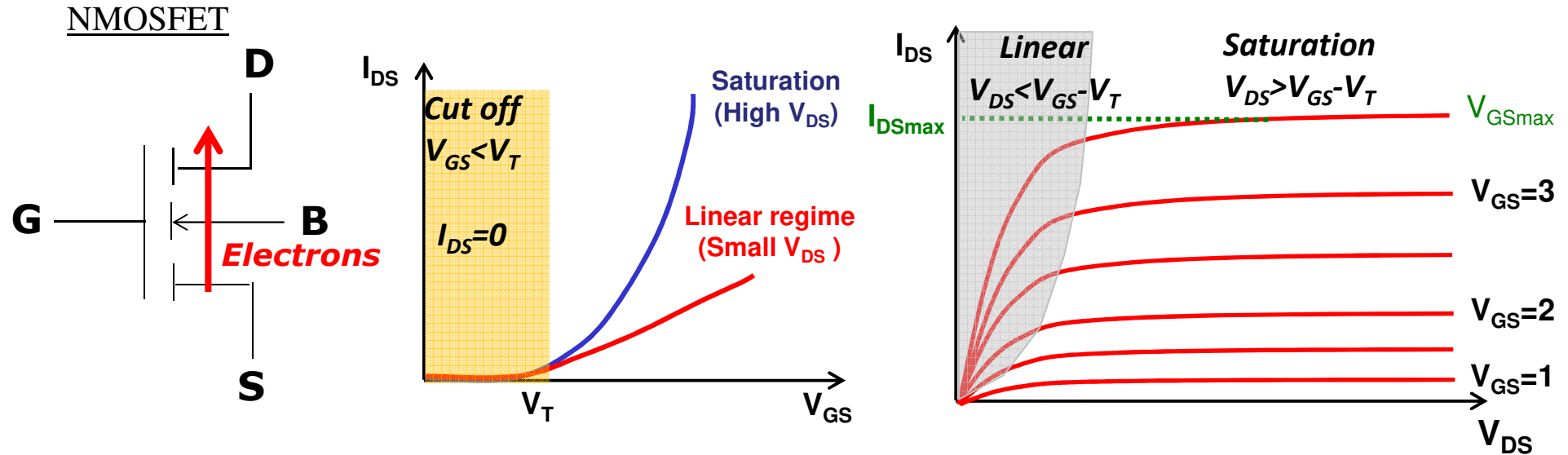


Static operating point (simplified model for long channel only)

**Linear regime ( $V_{DS} < V_{GS} - V_T$ ):** 
$$I_{DS} = K \left( (V_{GS} - V_T) \cdot V_{DS} - \frac{(V_{DS})^2}{2} \right) \times (1 + \lambda V_{DS})$$

**Saturation ( $V_{DS} > V_{GS} - V_T$ ):** 
$$I_{DS} = \frac{1}{2} K (V_{GS} - V_T)^2 \times (1 + \lambda V_{DS})$$

- In saturation,  $I_{DS}$  depends only on  $V_{GS}$
- Relationship between  $I_{DS}$  and  $V_{GS}$  is non-linear
- Equivalent to a voltage-controlled current source

## Simplified operation of MOSFET

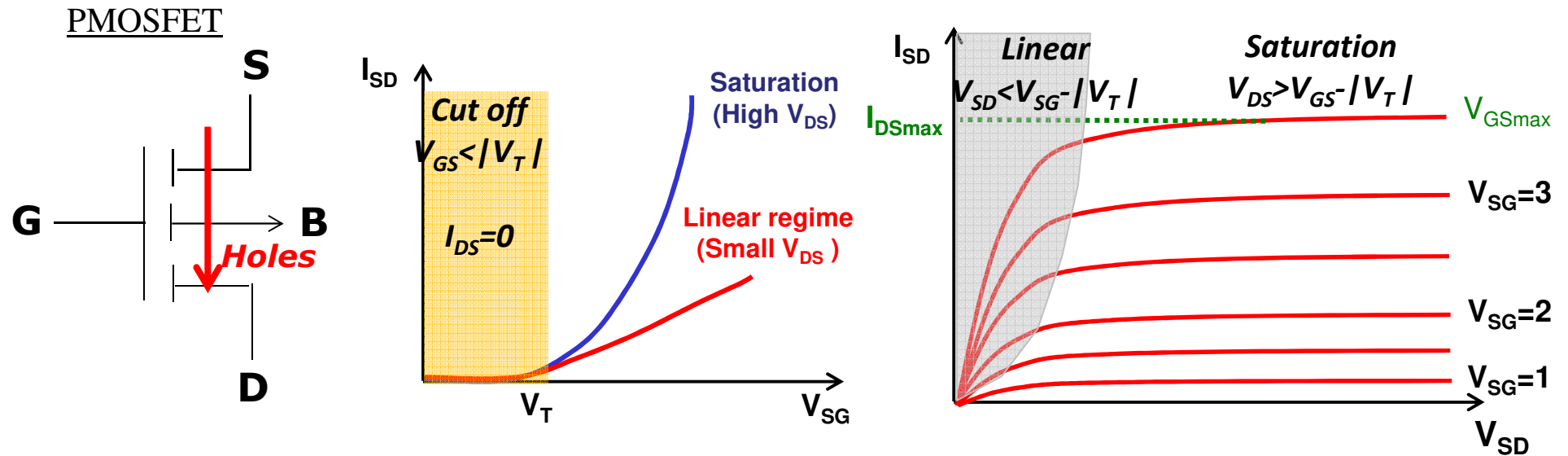

Static operating point (simplified model for long channel only)



**Linear regime ( $V_{SD} < V_{SG} - |V_T|$ ):** 
$$I_{sd} = K \left( (V_{sg} - |V_T|) \cdot V_{sd} - \frac{(V_{sd})^2}{2} \right) \times (1 + \lambda V_{sd})$$

**Saturation ( $V_{SD} > V_{SG} - |V_T|$ ):** 
$$I_{sd} = \frac{1}{2} K (V_{SG} - |V_T|)^2 \times (1 + \lambda V_{sd})$$

- In saturation,  $I_{DS}$  depends only on  $V_{GS}$
- Relationship between  $I_{DS}$  and  $V_{GS}$  is non-linear
- Equivalent to a voltage-controlled current source

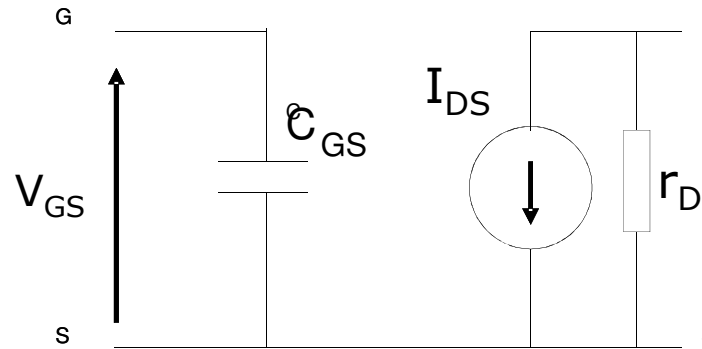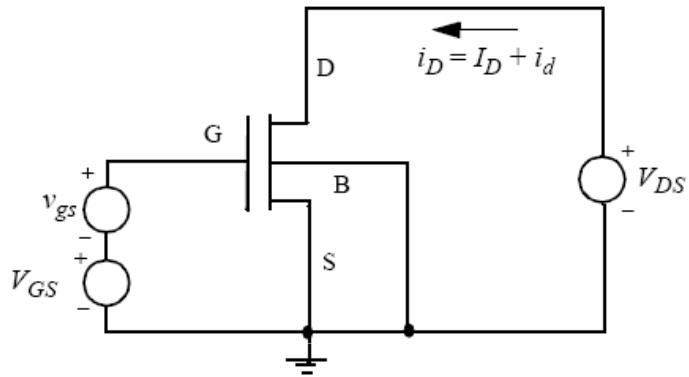
# Simplified small signal model (dynamic regime analysis)

In saturation regime ( $V_{DS} > V_{GS} - V_T$ ):



$$C_{gs} \approx \frac{2}{3} (WLC_{ox})$$

$$I_{ds} = g_m V_{gs}$$

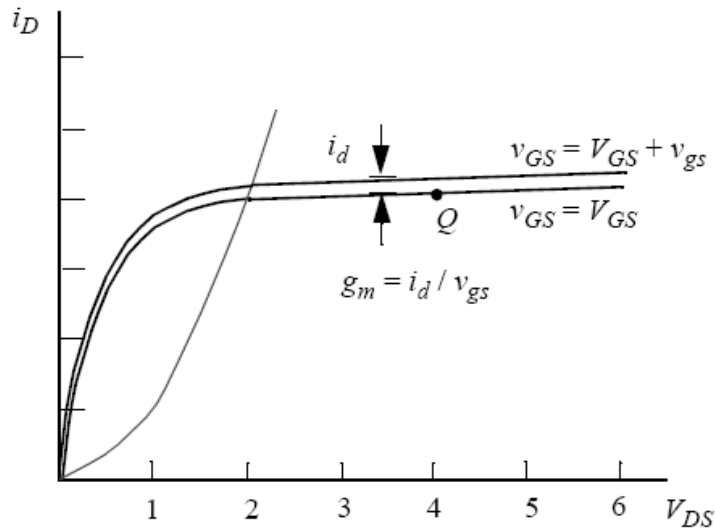

$$g_m \equiv \frac{\partial I_{DS}}{\partial V_{GS}} = K(V_{GS} - V_{Th})$$

$$g_m = UO \frac{\epsilon_0 \epsilon_r}{TOX} \cdot \frac{W}{L} (V_{GS} - V_{Th})$$

Fit by designer

The transconductance sets the voltage, current or power gain of amplifier stage

- Technology CMOS 0.35  $\mu\text{m}$  50 V (process H35B4S1)
- Integration on the same chip of power drivers (50 V) with command command and analog processing (3.3/5 V)
- Old technological node, but reliable, robust and low-cost technology → adapted to automotive industry
- Available devices (refer ENG-238\_rev6.pdf) :
  - NMOS/PMOSFET (LV and HV cores - 3.3 V à 50 V)
  - BJT vertical and lateral NPN/PNP
  - Diodes
  - Resistor (diffusion, Nwell, POLY1/2/H)
  - Capacitor (MIM, POLY, POLY-Metal)



- MOSFET

- List of available NMOSFET

MOSFET	HV CMOS core	5V gate	20V gate	NMOS50	Substrate logic	Isolated low VT
NMOS	x			x	x	
NMOS20H	x		x			
NMOS20HS	x		x			
NMOS20M	x	x				
NMOS20T	x					
NMOS50H	x		x	x		
NMOS50HS	x		x	x		
NMOS50M	x	x		x		
NMOS50T	x			x		
NMOSDI20H	x		x			
NMOSDI20M	x	x				
NMOSDI50H	x		x			
NMOSH	x			x	x	
NMOSI	x					
NMOSI20H	x		x			
NMOSI20M	x	x				
NMOSI20T	x					
NMOSI50H	x		x			
NMOSI50M	x	x				
NMOSI50T	x					
NMOSIL	x					x
NMOSIM	x	x				
NMOSIML	x	x				x
NMOSM	x	x		x	x	
NMOSMH	x	x		x	x	



- ✓ Nominal voltage: 3.3 V, 5 V, 20 V, 50 V ( $V_{gs}$ ,  $V_{ds}$ ,  $V_{db}$ )
- ✓ Isolated and non-isolated version

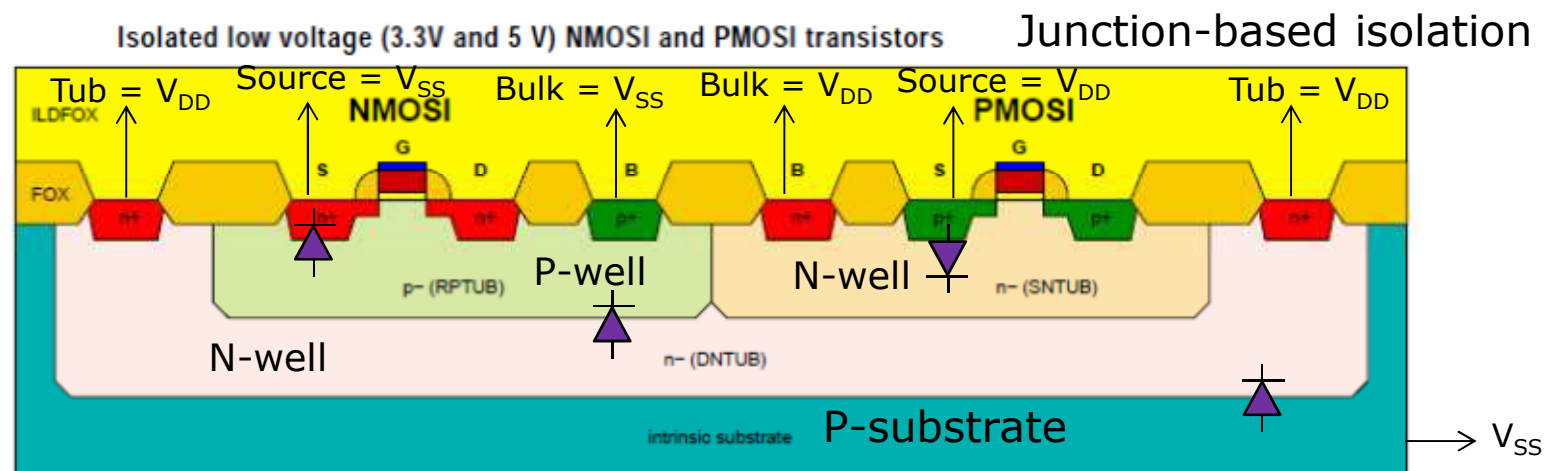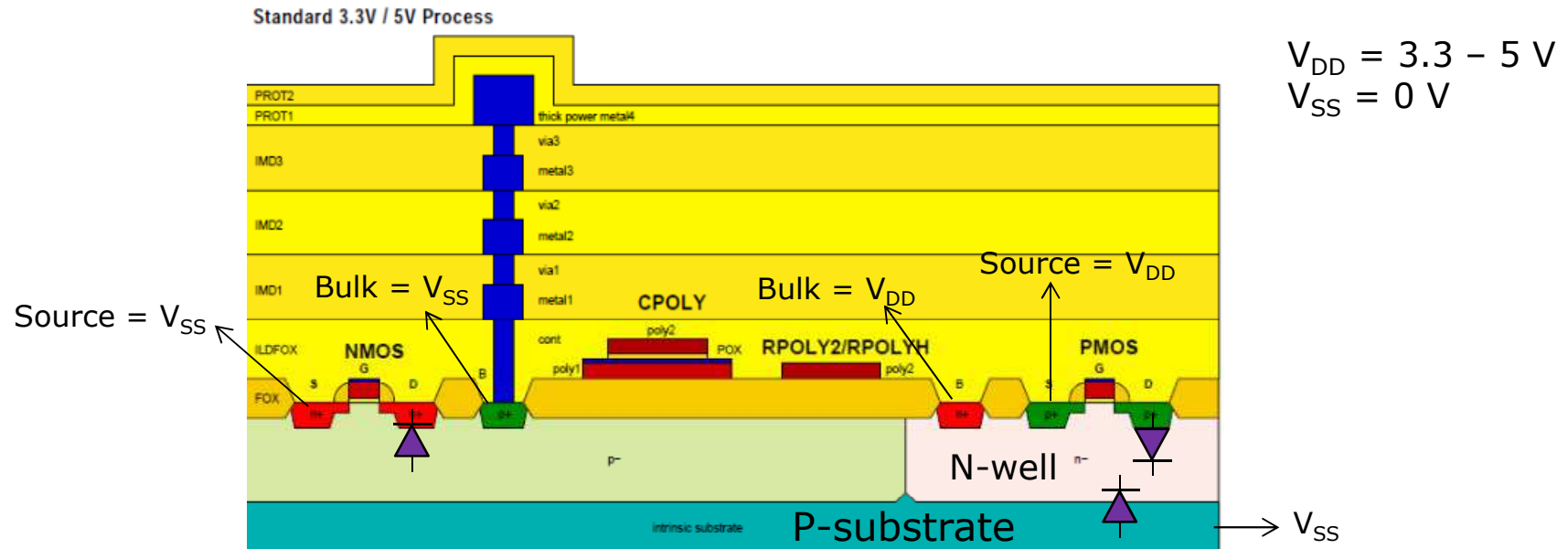- MOSFET – Wafer cross-section (ENG-236\_rev6.pdf)



- MOSFET – Wafer cross-section (ENG-236\_rev6.pdf)

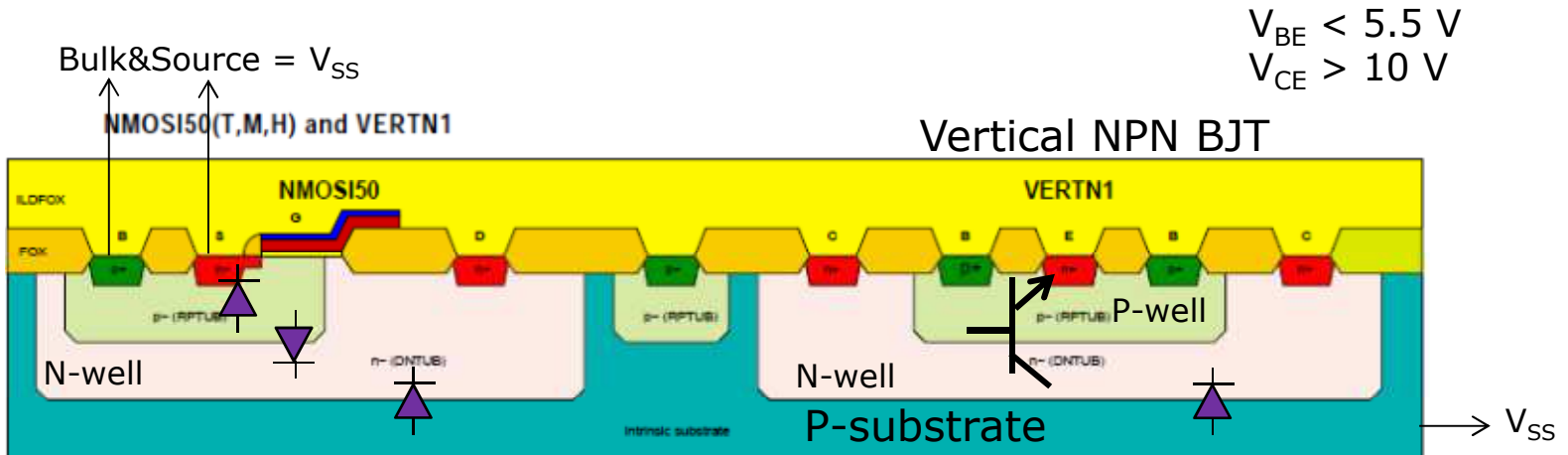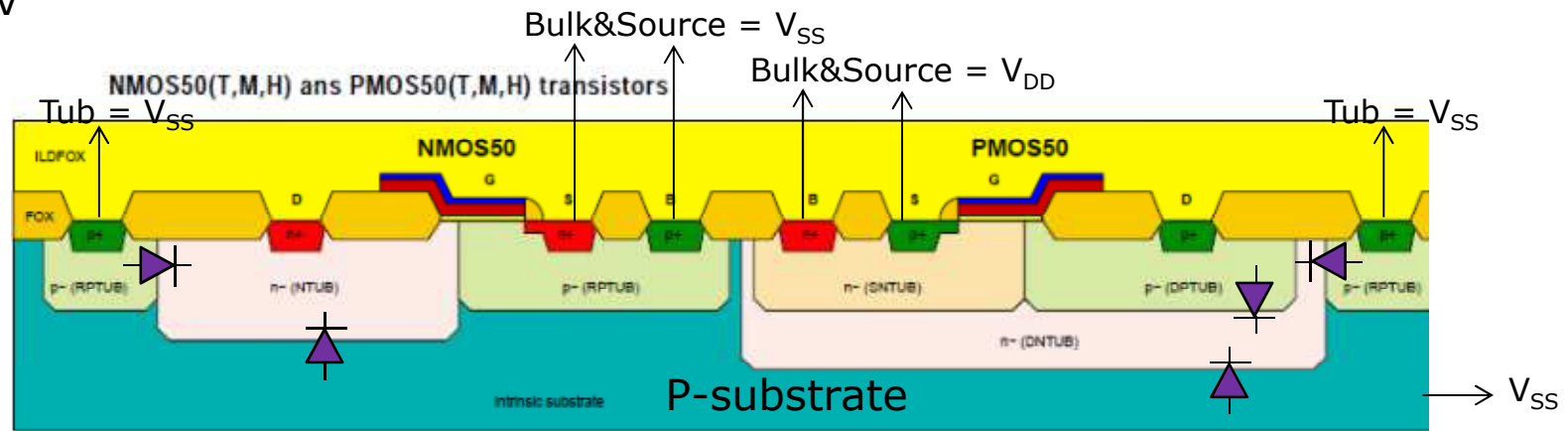
$V_{DD} < 50\text{ V}$   
 $V_{SS} = 0\text{ V}$



$V_{BE} < 5.5\text{ V}$   
 $V_{CE} > 10\text{ V}$



## CMOS power driver (half-bridge)

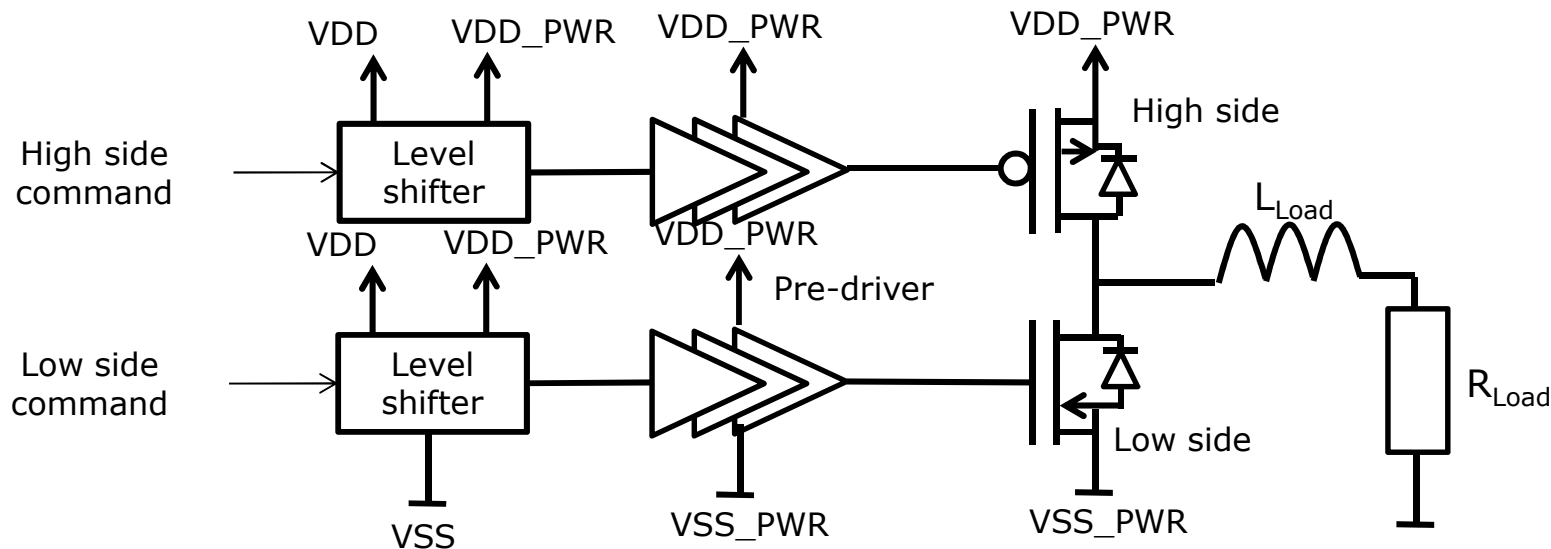

- Constraints :
  - Efficiency optimization (reduce power losses)
  - Small  $R_{on}$  → small drain-source voltage drop → reduction of power dissipation
  - Dead time (remove « crossbar current » or « shoot-through current »)
  - Robustness to overvoltage
  - Slew rate control (EMC)


## CMOS power driver (half-bridge)

- Smart Power IC example (High Voltage CMOS 0.35  $\mu\text{m}$ ) –  $I_{\text{max}} = 1 \text{ A}$

High side  
( $W=9500 \mu\text{m}$ ,  
 $L= 0.7 \mu\text{m}$ )


Low side  
( $W=7000 \mu\text{m}$ ,  
 $L= 0.7 \mu\text{m}$ )

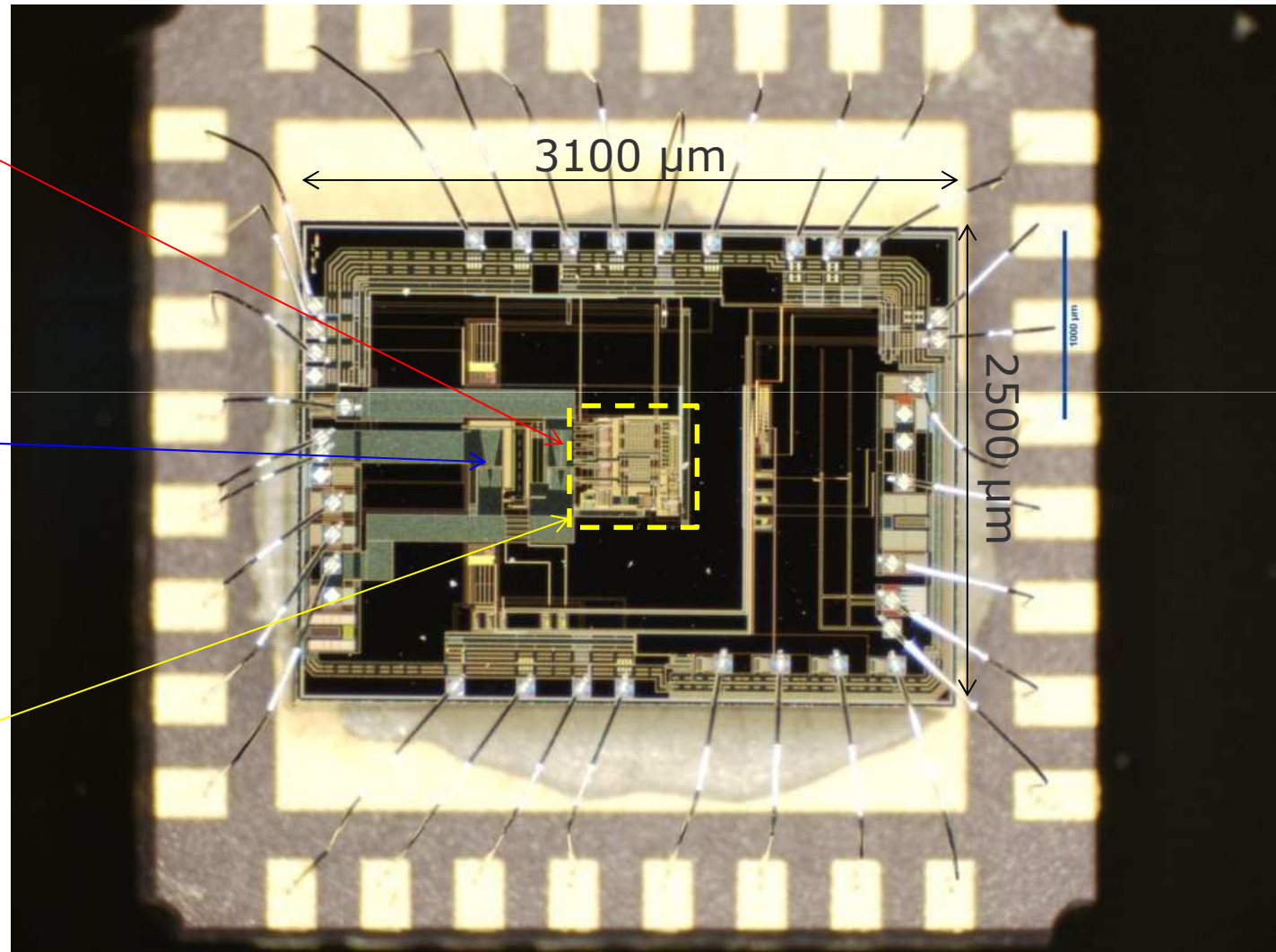Command +  
pre-driver +  
on-chip  
diagnosis



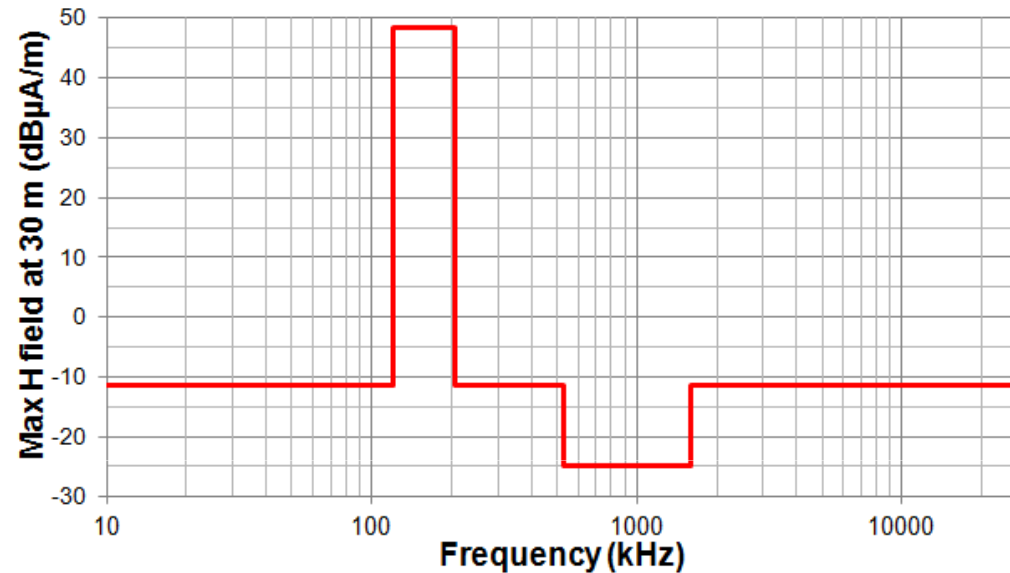
## CMOS power driver (half-bridge)

- EMC constraints: maximum magnetic field H emission (EN55011)



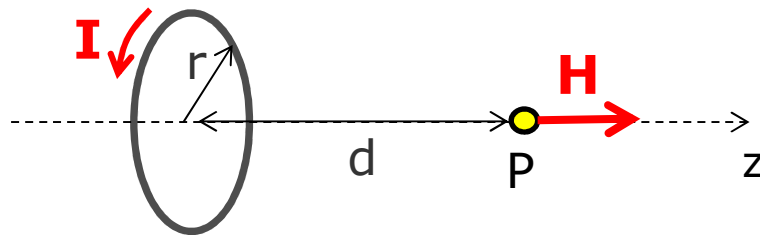
- Magnetic field emission model derived from a N turn small circular loop excited by a constant current



$$H \text{ (A/m)} = \frac{Nr^2 I}{2(r^2 + d^2)^{3/2}}$$

## Basic coupling model between primary and secondary coils

- Equivalent electrical model:

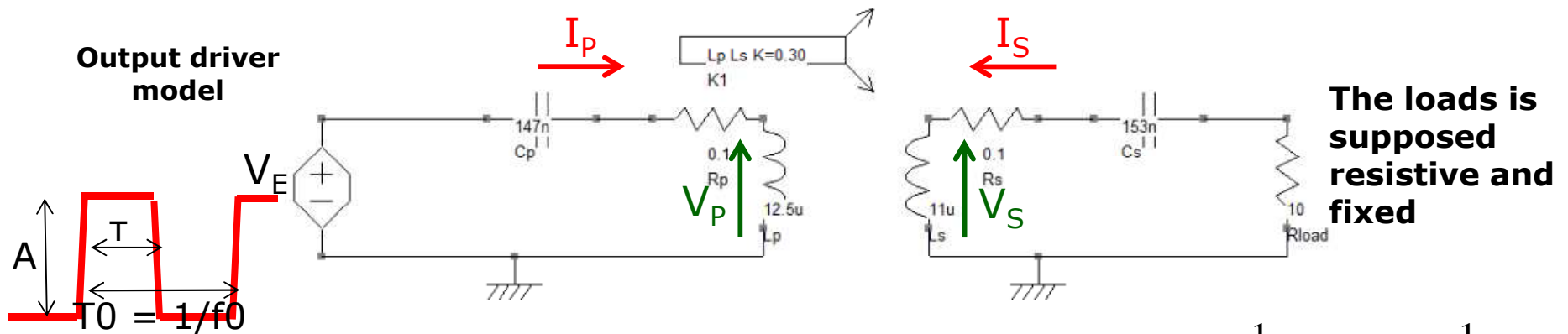

- Inductive coupling coefficient:
- Harmonic analysis:

$$k = \frac{M}{\sqrt{L_P L_S}} \quad f_{res} = \frac{1}{2\pi\sqrt{L_P C_P}} = \frac{1}{2\pi\sqrt{L_S C_S}}$$

$$\begin{cases} v_{L_P} = jL_P \omega i_p + jM \omega i_s \\ v_{L_S} = jL_S \omega i_s + jM \omega i_p \end{cases} \quad \longrightarrow \quad I_S = \frac{-jM\omega}{M^2\omega^2 + Z_P Z_S} V_E \quad I_P = \left(1 - \frac{M^2\omega^2}{M^2\omega^2 + Z_P Z_S}\right) \frac{V_E}{Z_P}$$

Avec :  $Z_P = R_P + jL_P\omega + \frac{1}{jC_P\omega}$        $Z_S = R_{Load} + R_S + jL_S\omega + \frac{1}{jC_S\omega}$



- First harmonic assumption:

Square signal command  $|V_E(nf_0)| = \frac{2A\tau}{T_0} \left| \frac{\sin\left(\frac{n\pi\tau}{T_0}\right)}{\frac{n\pi\tau}{T_0}} \right| \quad \longrightarrow \quad |V_E(f_0)| = \frac{2A}{\pi} \quad si \tau = \frac{T_0}{2}$



## Basic coupling model between primary and secondary coils

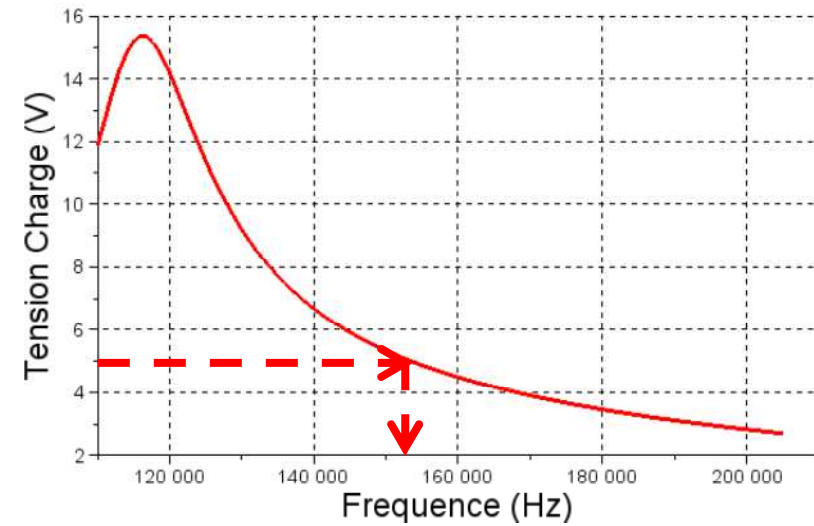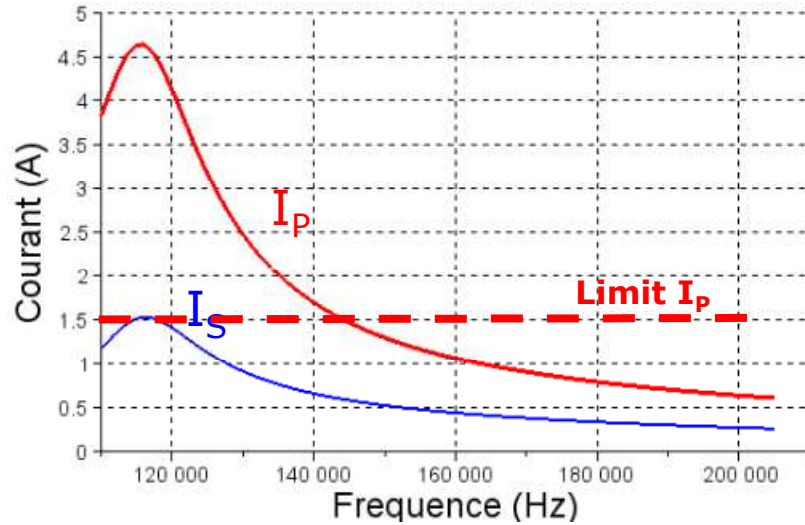- Example :**

$F_{res} = 117 \text{ kHz}$ ,  $\tau = T_0/2$ ,  $A = 9 \text{ V}$ ,  $k = 0.4$ ,  $R_L = 10 \Omega$





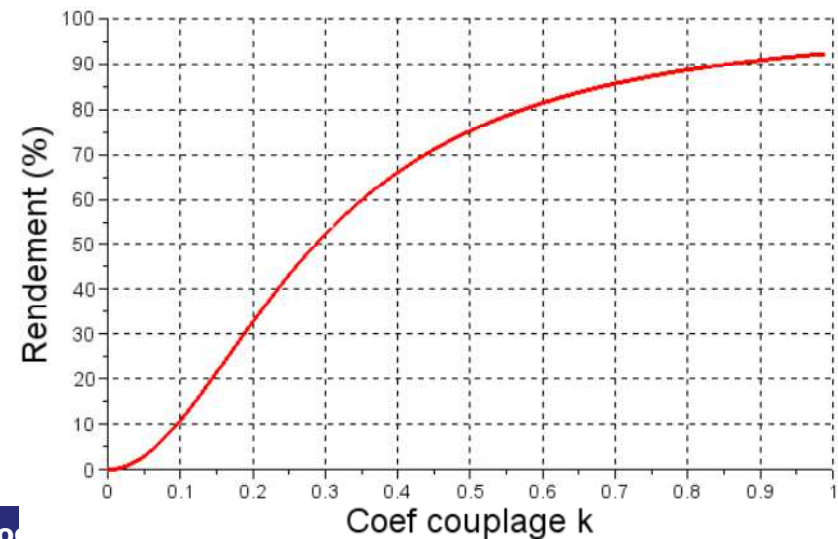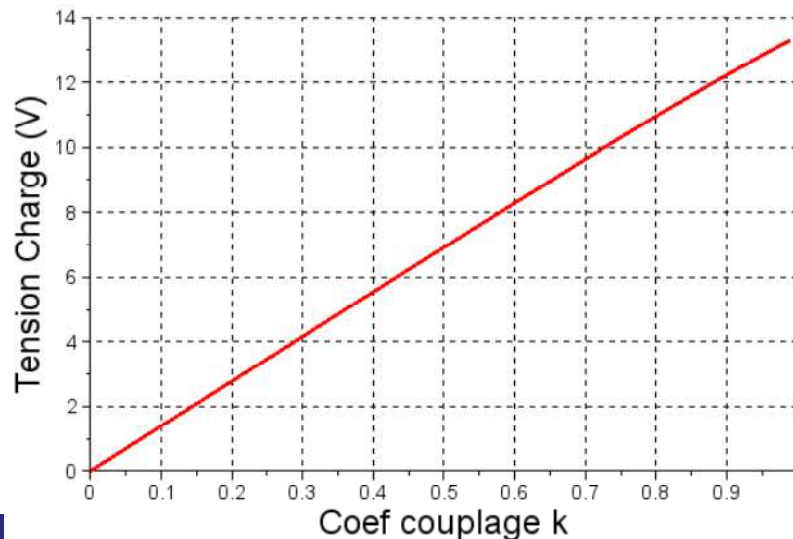$F_{res} = 117 \text{ kHz}$ ,  $F_0 = 150 \text{ kHz}$ ,  $\tau = T_0/2$ ,  $A = 9 \text{ V}$ ,  $R_L = 10 \Omega$





- Some elementary analog structures

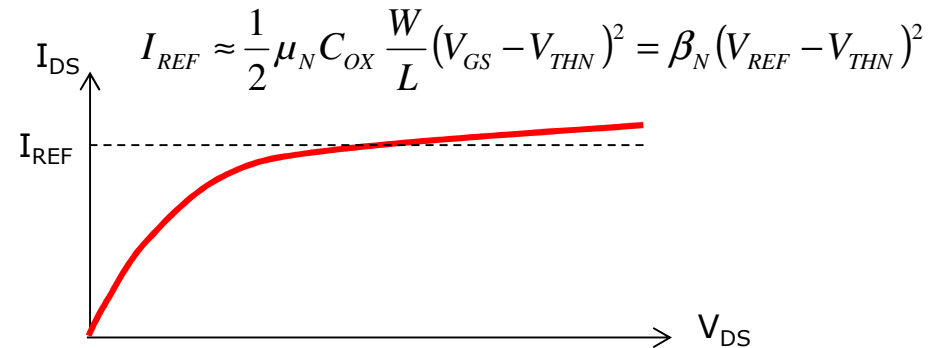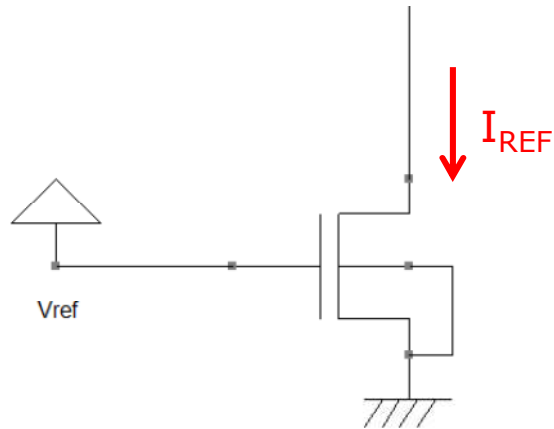Current source (basically, a NMOSFET or PMOSFET in saturation)




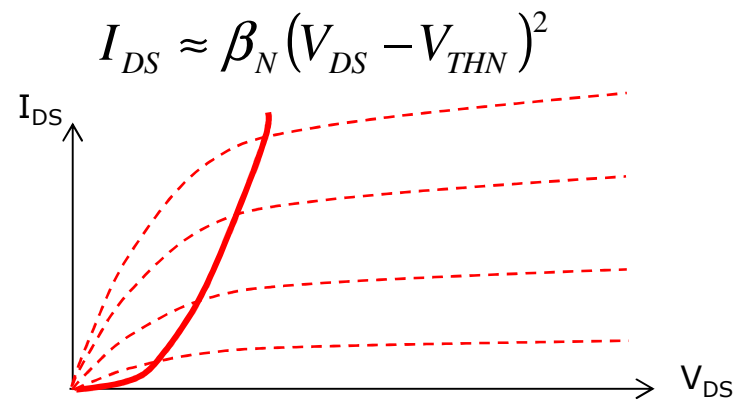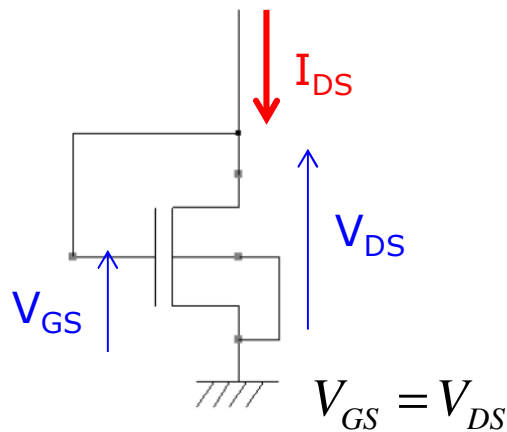MOSFET-based diode (Active load → compact load)



- Some elementary analog structures

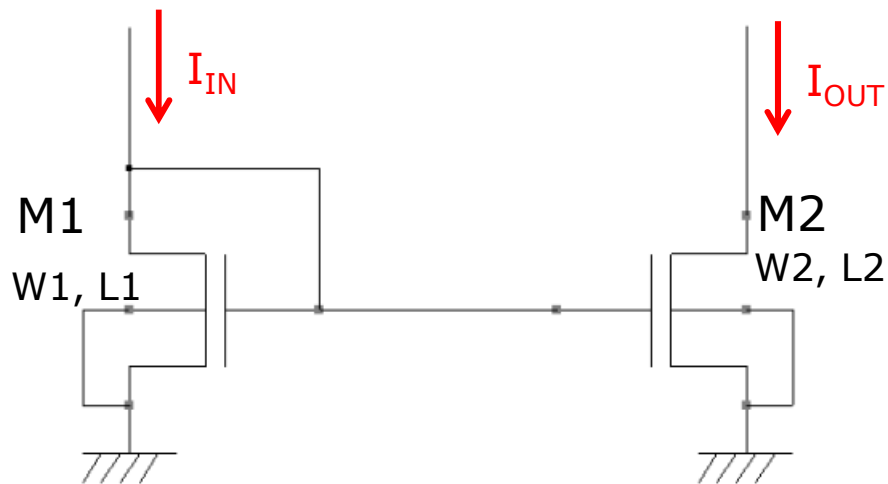Current mirror (based on NMOSFET or PMOSFET)




M1 and M2 have same characteristics, except dimensions  $W$  and  $L$  which can be different


$$\frac{W_2}{L_2} = K \frac{W_1}{L_1}$$

If M2 is in saturation and if its output conductance is null:

$$I_{OUT} = K \times I_{IN}$$

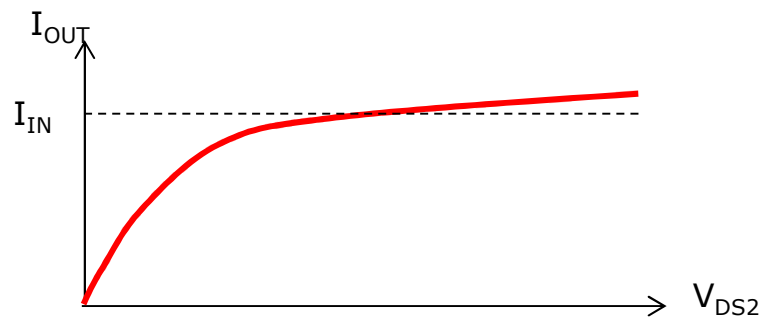


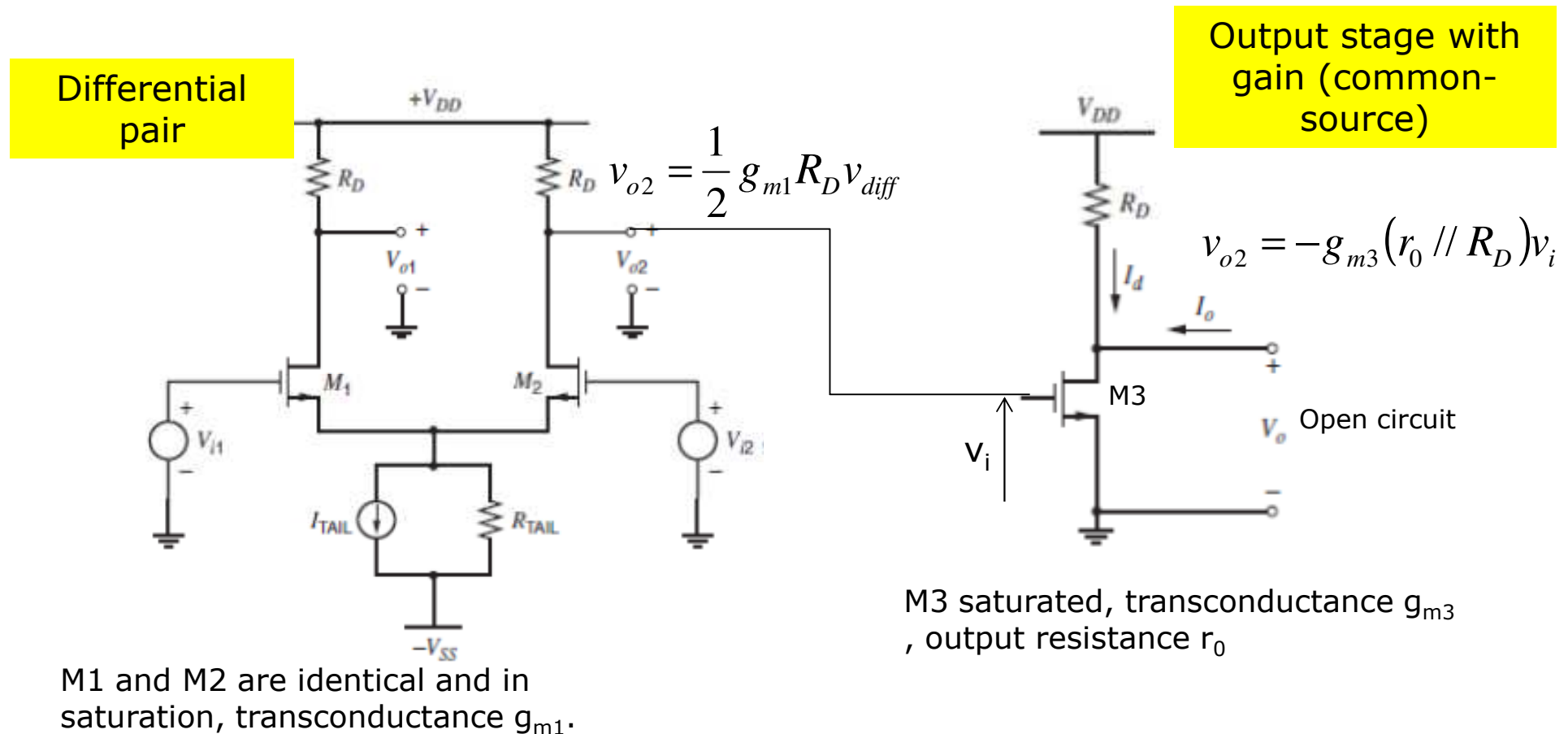- Refer to book Gray, Hurst, Lewis, Meyer, « Analysis and Design of Analog Integrated Circuits », chapitres 6, 7, 8
- Principle of two-stage diff. Amplifier with single-ended output:







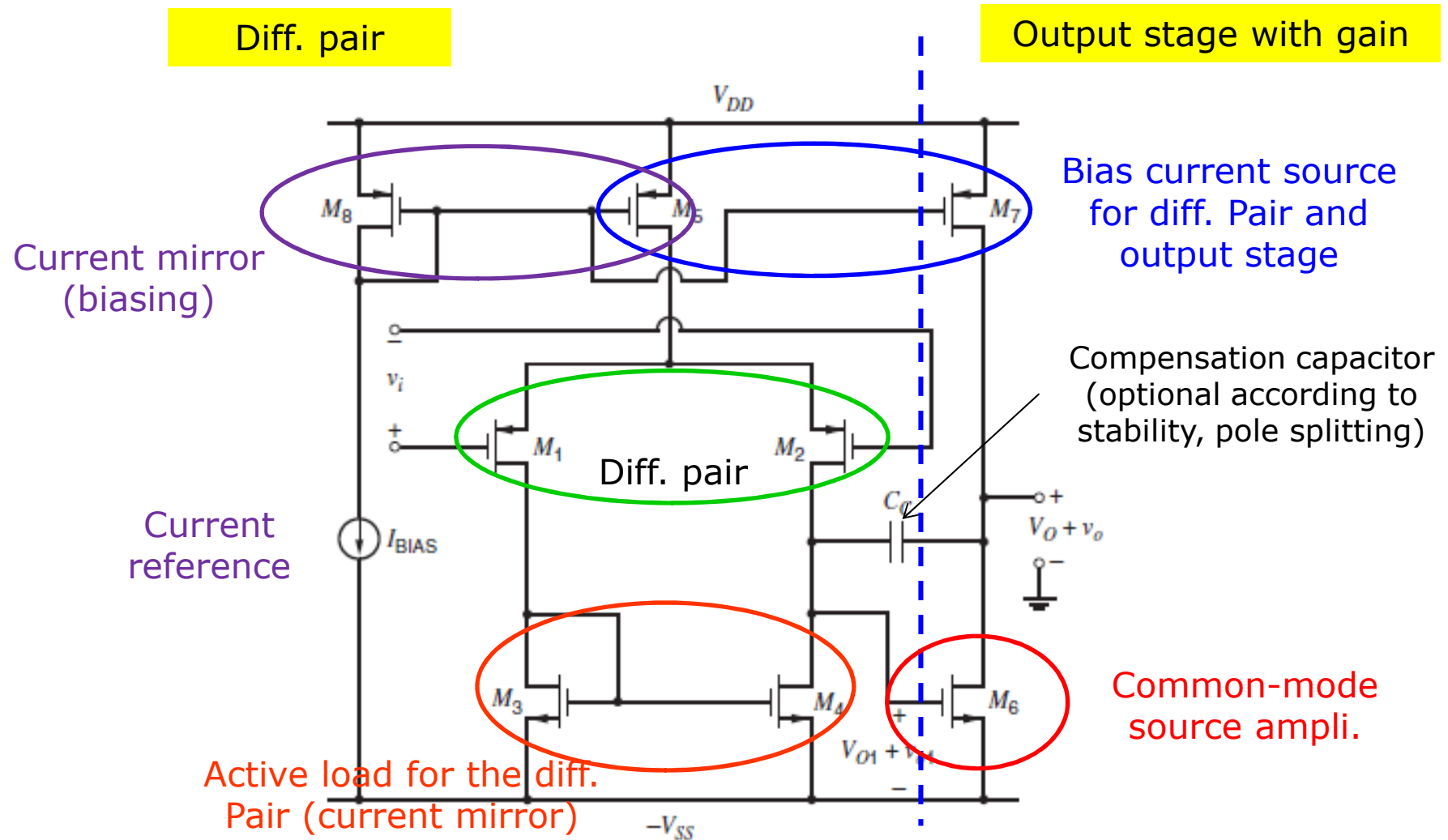- Miller OTA amplifier (with PMOSFET diff. pair):



- Main characteristics to control:
  - Tatic gain
  - Output voltage range (rail-to-rail ideally)
  - Input/output offset
  - Common-mode rejection
  - Bandwidth, gain-bandwidth product
  - Open-loop transfer function, poles, stability (phase margin)
  - Slew rate
  - Power supply rejection ratio (PSRR)
  - Power consumption

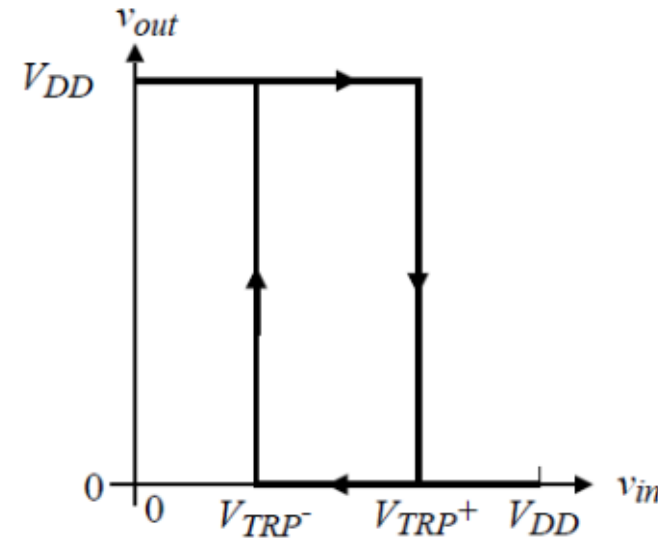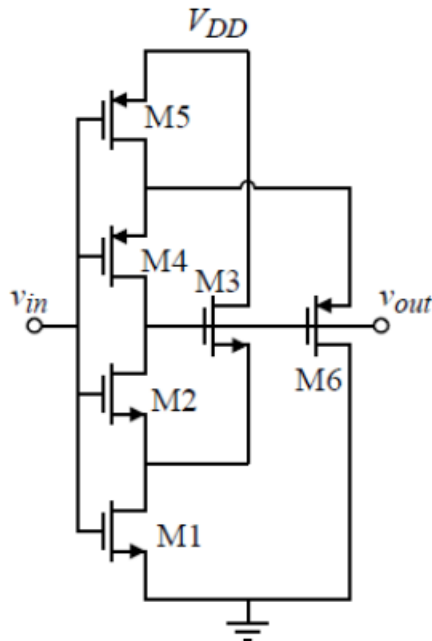- OPA based comparator (slew rate, offset issues...)
- Schmitt trigger (digital structure):



$$V_{TRP^-} = \frac{\sqrt{\beta_5/\beta_6} (V_{DD} - V_{TP5})}{1 + \sqrt{\beta_5/\beta_6}}$$


$$V_{TRP^+} = \frac{V_{TN1} + \sqrt{\beta_3/\beta_1} V_{DD}}{1 + \sqrt{\beta_3/\beta_1}}$$

With :

- ✓  $V_{Txx}$  = Threshold voltage ( $V_{TN2} = V_{TN3}$ ,  $V_{TP4} = V_{TP6}$ )
- ✓  $\beta_x = \frac{1}{2} \mu_x C_{ox} W/L$  = transconductance



- Example: current reference

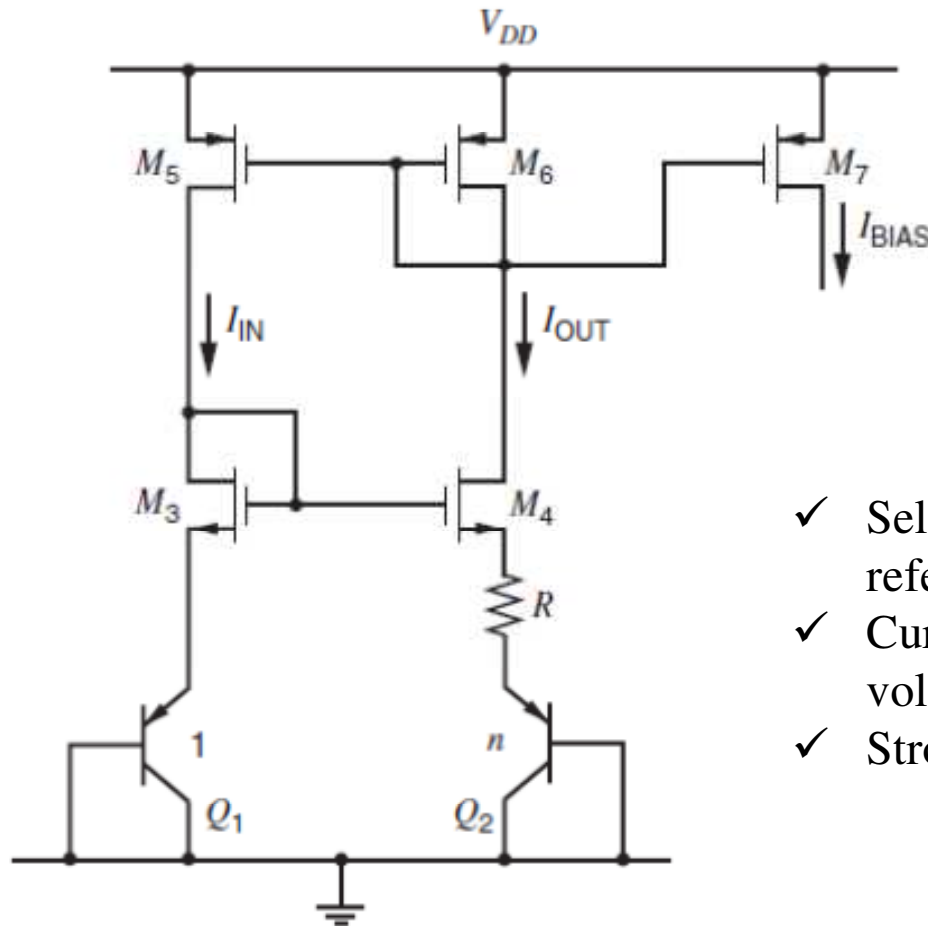

If  $M3 = M4$  et  $M5 = M6$  and in saturation :

✓  $I_{IN} = I_{OUT}$


✓ 
$$I_{OUT} = \frac{kT}{q} \frac{\ln(n)}{R}$$

✓ If  $M7 = M6$ ,  $I_{BIAS} = I_{OUT}$

- ✓ Self-biased structure (no external current reference is required)
- ✓ Current weakly dependent on power supply voltage
- ✓ Strong dependence to temperature

## Temperature impact

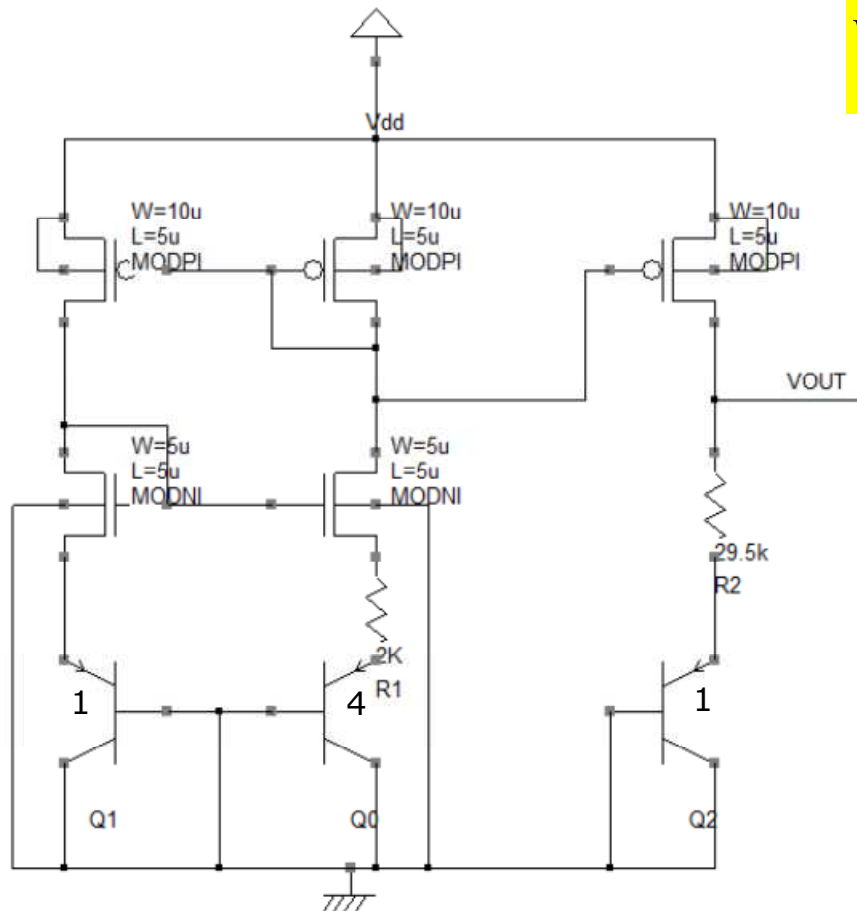- Example: bandgap voltage reference
- Reuse the previous current reference and adding of a temperature compensation strategy



$$V_{OUT} = V_{EB2} + R_2 I_{OUT} = V_{EB2} + R_2 \frac{kT \ln(n)}{q R}$$


- ✓ Proportional To Absolute Temperature (PTAT) = voltage drop across R2 ( $dV_{R2}/dT \approx +1.8 \text{ mV}/^\circ \text{ c}$ )
- ✓ Complementary To Absolute Temperature (CTAT) = PNP-based diode ( $dV_{EB}/dT \approx -2 \text{ mV}/^\circ \text{ c}$ )



VBE multiplier
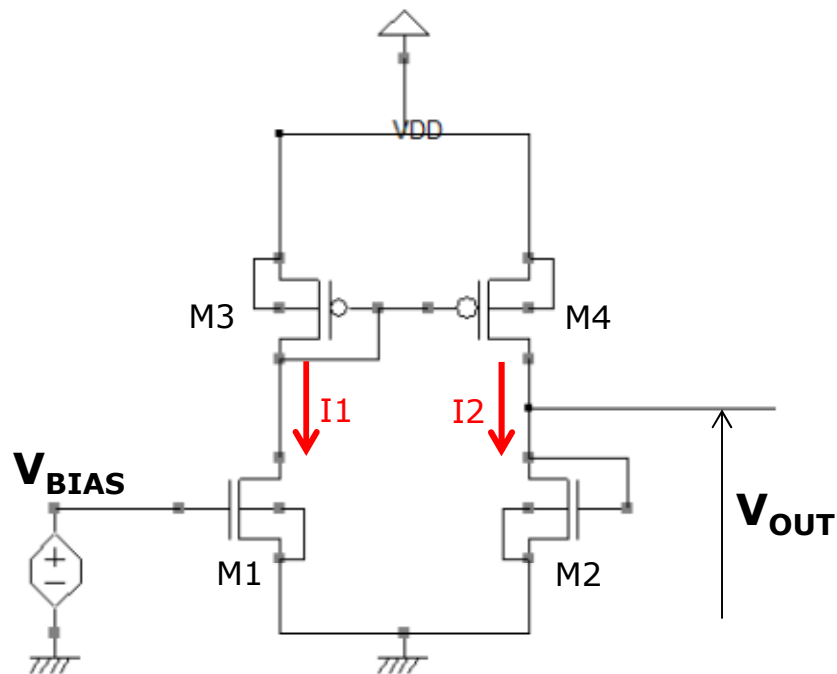
## Temperature impact

- Fully CMOS temperature sensor: based on temperature dependence of  $V_{TH}$



$$V_{TH} \approx V_{TH0} + \alpha(T - T_0), \alpha = -0.5 \dots -2 \text{ mV} / ^\circ\text{C}$$

- ✓ M1, M2, M3, M4 in saturation
- ✓ If M3 = M4  $\rightarrow I_1 = I_2$  (current mirror)
- ✓  $V_{TH1} = V_{TH2}$


- ✓ M2 is mounted as a diode:

$$V_{OUT} = V_{GS2} = \sqrt{\frac{I_2}{\beta_2}} + V_{TH2}$$

- ✓ M1 controlled by  $V_{bias} \rightarrow$  set the bias current :

$$I_1 = \beta_1 (V_{BIAS} - V_{TH1})^2$$
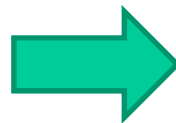
$$V_{OUT} = \sqrt{\frac{\beta_1}{\beta_2}} V_{BIAS} + V_{TH} \left( 1 - \sqrt{\frac{\beta_1}{\beta_2}} \right)$$



$$V_{TH} = \frac{V_{OUT} - \sqrt{\frac{\beta_1}{\beta_2}} V_{BIAS}}{1 - \sqrt{\frac{\beta_1}{\beta_2}}}$$